


DIGITAL LOGIC DESIGN LAB (EET1211)

LAB I: Examine the Operation of Logic Gates Using HDL

Siksha 'O' Anusandhan Deemed to be University, Bhubaneswar

Branch:		Section:	
S. No.	Name	Registration No.	Signature
	Deepak Pattnayak	1941012112	

Marks: ____/10

Remarks:

Teacher's Signature

I. OBJECTIVE:

1. Investigation of the logic behavior of various gates using HDL:

- a) 7400 quadruple two-input NAND gates
- b) 7402 quadruple two-input NOR gates
- c) 7404 hex inverters
- d) 7408 quadruple two-input AND gates
- e) 7432 quadruple two-input OR gates
- f) 7486 quadruple two-input XOR gates

2. Using a single 7400 IC, connect and implement a circuit using HDL that produces

- a) An inverter.**
- b) A two-input AND.
- c) A two-input OR.
- d) A two-input XOR.

3. Construct & record the output of circuit using HDL that implements the Boolean function:



$$F=A (B+C)$$

- a) Construct the circuit using Logic gates & verify the truth table.
- b) Construct the circuit using NAND gates only & verify the truth table.

II. PRE-LAB


1. Draw the IC diagram & obtain truth tables for obj. 1-

- a. 7400 2 Input NAND Gate

 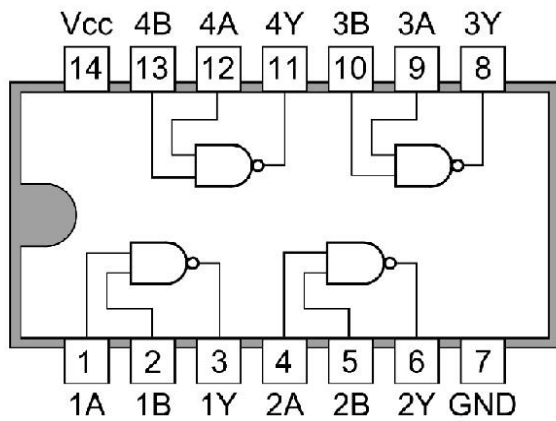


INPUT		OUTPUT
A	B	
0	0	1
1	0	1
0	1	1
1	1	0

b. 7402 2 Input NOR Gate


 


Connection Diagram

 


INPUT		OUTPUT
A	B	
0	0	1
1	0	0
0	1	0
1	1	0

c. 7404 Hex Inverter

 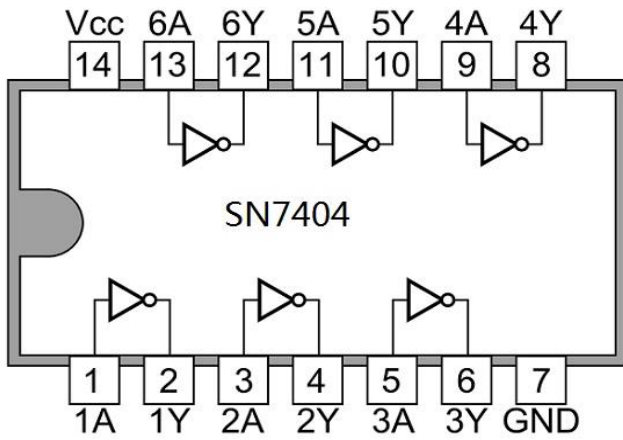


INPUT		OUTPUT
A		
0		1
1		0

d. 7408 2 Input AND Gate

 


INPUT		OUTPUT
A	B	
0	0	0
1	0	0
0	1	0
1	1	1

e. 7432 2 Input OR GATE

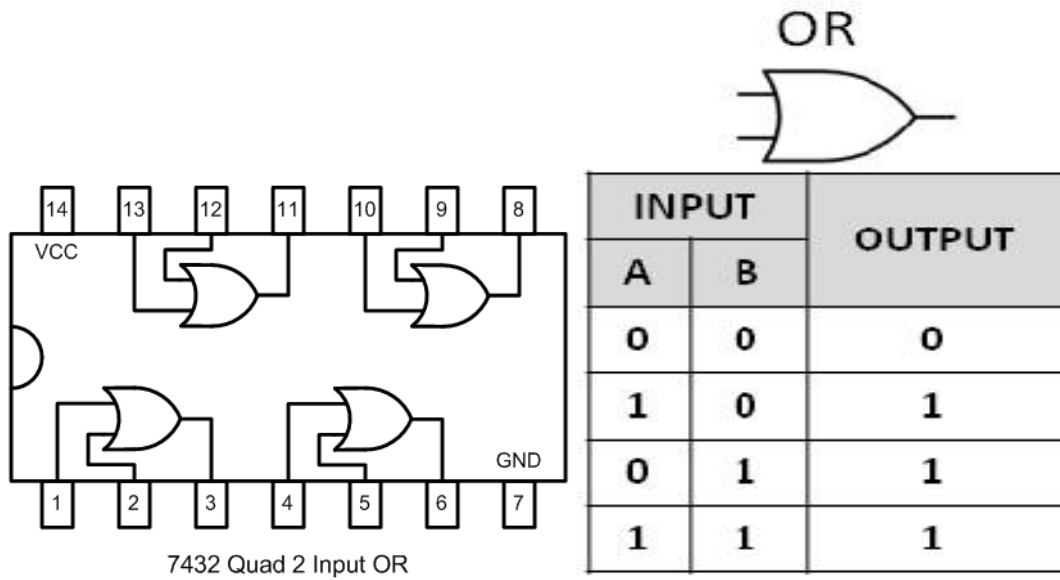


f. 7486 2 Input XOR

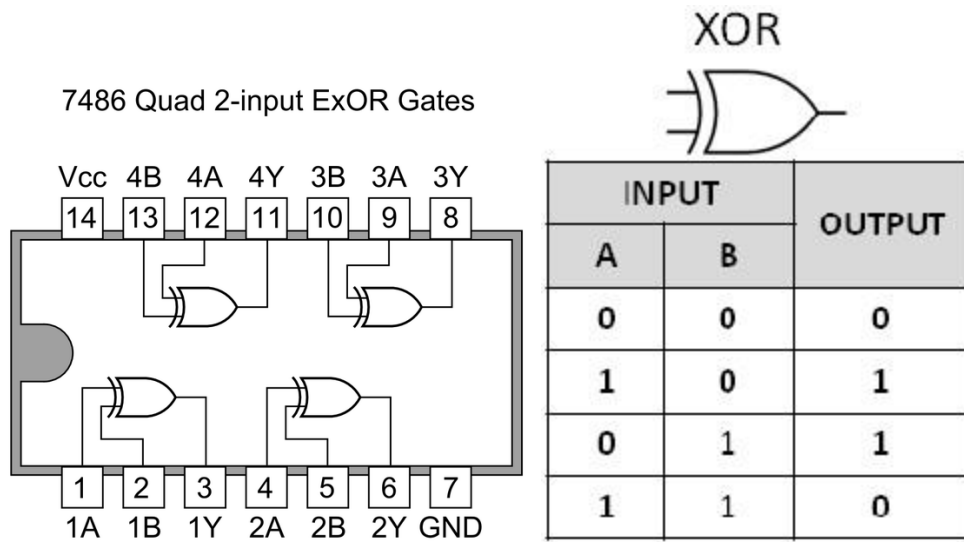

2. Draw the circuit diagram & obtain truth tables for obj. 2 & 3-


a) An inverter.

Truth Table

 


A	$Q = \overline{A.A}$
0	1
1	0

b) A two-input AND.

 

Truth Table			
A	B	$C = \overline{A.B}$	$Q = \overline{C.C}$
0	0	1	0
0	1	1	0
1	0	1	0
1	1	0	1


c) A two-input OR.

 

Truth Table				
A	B	$C = \overline{A.A}$	$D = \overline{B.B}$	$Q = \overline{C.D}$
0	0	1	1	0
0	1	1	0	1
1	0	0	1	1
1	1	0	0	1

A	B	$C = \overline{A.B}$	$D = \overline{A.C}$	$E = \overline{B.C}$	$Q = \overline{D.E}$
0	0	1	1	1	0
0	1	1	1	0	1


d) A two-input XOR.

 

1	0	1	0	1	1
1	1	0	1	1	0

3

 
a) Construct the circuit using Logic gates & verify the truth table.



Truth Table				
A	B	C	B+C	F=A(B+C)
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	1	0
1	0	0	0	0
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

b) Construct the circuit using NAND gates only & verify the truth table.

Truth Table							
A	B	C	$X=\overline{B.B}$	$Y=\overline{C.C}$	$Z=\overline{X.Y}$	$P=\overline{A.Z}$	$F=\overline{P.P}$

 

0	0	0	1	1	0	1	0
0	0	1	1	0	1	1	0
0	1	0	0	1	1	1	0
0	1	1	0	0	1	1	0
1	0	0	1	1	0	1	0
1	0	1	1	0	1	0	1
1	1	0	0	1	1	0	1
1	1	1	0	0	1	0	1

III. LAB:

HDL Program:

1. a) 7400 quadruple two-input NAND gate

design.sv

```
`default_nettype none

module input_2_nand (
    input A,B,
    output X
);

    nand(X,A,B); //GATE LEVEL
    assign X = !(A && B); //DATAFLOW

endmodule
```

testbench.sv

```
`default_nettype none

module nand_2input;

    reg i_a,i_b;
    wire out_x;

    input_2_nand h_dut(i_a,i_b,out_x);

    // UPDATED UNIT TEST //

    initial
        begin
            $dumpfile("dump.vcd");
            $dumpvars(0, h_dut);

            $display("TESTING nand example");
            #1
            i_a <= 0;
            i_b <= 0;
            #1

            #1
            i_a <= 0;
            i_b <= 1;
            #1

            #1
```

```

    i_a <= 1;
    i_b <= 0;
    #1

    #1
    i_a <= 1;
    i_b <= 1;
    #1

    $finish();
end

```

endmodule

LINK: <https://www.edaplayground.com/x/TRFA>

b) 7402 quadruple two-input NOR gate

design.sv

```
`default_nettype none
```

```

module input_2_nor (
    input A,B,
    output X
);

    nor(X,A,B); //GATE LEVEL
    assign X = !(A || B); //DATAFLOW

endmodule

```

testbench.sv

```
`default_nettype none
```

```

module nor_2input;

    reg i_a,i_b;
    wire out_x;

    input_2_nor h_dut(i_a,i_b,out_x);

    // UPDATED UNIT TEST //

```

```

initial
begin
    $dumpfile("dump.vcd");
    $dumpvars(0, h_dut);

    $display("TESTING nor example");
    #1
    i_a <= 0;
    i_b <= 0;
    #1

    #1
    i_a <= 0;
    i_b <= 1;
    #1

    #1
    i_a <= 1;
    i_b <= 0;
    #1

    #1
    i_a <= 1;
    i_b <= 1;
    #1

    $finish();
end

endmodule

```

LINK: <https://www.edaplayground.com/x/6rdY>

c) 7404 hex inverters

design.sv

```
`default_nettype none
```

```

module hex_inverter (
    input A,
    output X
);

```

```
not(X,A); //GATE LEVEL
assign X = ~A; //DATAFLOW
```

```
endmodule
```

testbench.sv

```
`default_nettype none

module inverter_x;

    reg i_a;
    wire out_x;

    hex_inverter h_dut(i_a,out_x);

    // UPDATED UNIT TEST //

    initial
        begin
            $dumpfile("dump.vcd");
            $dumpvars(0, h_dut);

            $display("TESTING hex-inverter example");
            #1
            i_a <= 0;
            #1

            #1
            i_a <= 1;
            #1
            $finish();
        end

endmodule
```

LINK: <https://www.edaplayground.com/x/sALM>

d) 7408 quadruple two-input AND gates

design.sv

```
`default_nettype none
```

```
module input_2_and (  
    input A,B,  
    output X  
);  
  
    and(X,A,B); //GATE LEVEL  
    assign X = (A && B); //DATAFLOW  
  
endmodule
```

testbench.sv

```
`default_nettype none
```

```
module and_2input;  
  
    reg i_a,i_b;  
    wire out_x;  
  
    input_2_and h_dut(i_a,i_b,out_x);  
  
    // UPDATED UNIT TEST //  
  
    initial  
    begin  
        $dumpfile("dump.vcd");  
        $dumpvars(0, h_dut);  
  
        $display("TESTING and example");  
        #1  
        i_a <= 0;  
        i_b <= 0;  
        #1  
  
        #1  
        i_a <= 0;  
        i_b <= 1;  
        #1  
  
        #1  
        i_a <= 1;
```

```

        i_b <= 0;
        #1

        #1
        i_a <= 1;
        i_b <= 1;
        #1

        $finish();
    end

endmodule

```

LINK: <https://www.edaplayground.com/x/dg3V>

e) 7432 quadruple two-input OR gates

design.sv

```

`default_nettype none

module input_2_or (
    input A,B,
    output X
);

    or(X,A,B); //GATE LEVEL
    assign X = (A || B); //DATAFLOW

endmodule

```

testbench.sv

```

`default_nettype none

module or_2input;

    reg i_a,i_b;
    wire out_x;

    input_2_or h_dut(i_a,i_b,out_x);

    // UPDATED UNIT TEST //

    initial
        begin

```

```
$dumpfile("dump.vcd");
$dumpvars(0, h_dut);
```

```
$display("TESTING or example");
```

```
#1
i_a <= 0;
i_b <= 0;
#1
```

```
#1
i_a <= 0;
i_b <= 1;
#1
```

```
#1
i_a <= 1;
i_b <= 0;
#1
```

```
#1
i_a <= 1;
i_b <= 1;
#1
```

```
$finish();
end
```

```
endmodule
```

LINK: <https://www.edaplayground.com/x/mr7G>

f) 7486 quadruple two-input XOR gates

design.sv

```
`default_nettype none
```

```
module input_2_xor (
    input A,B,
    output X
);
```

```
xor(X,A,B); //GATE LEVEL
assign X = ~A&&B || A&&~B; //DATAFLOW
```

```
endmodule
```

testbench.sv

```
`default_nettype none
module xor_2input;

    reg i_a,i_b;
    wire out_x;

    input_2_xor h_dut(i_a,i_b,out_x);

    // UPDATED UNIT TEST //

    initial
    begin
        $dumpfile("dump.vcd");
        $dumpvars(0, h_dut);

        $display("TESTING xor example");
        #1
        i_a <= 0;
        i_b <= 0;
        #1

        #1
        i_a <= 0;
        i_b <= 1;
        #1

        #1
        i_a <= 1;
        i_b <= 0;
        #1

        #1
        i_a <= 1;
        i_b <= 1;
        #1

        $finish();
    end

endmodule
```

LINK: <https://www.edaplayground.com/x/tmfW>

2.a) Using a single 7400 IC as an Inverter

design.sv

```
`default_nettype none

module NAND_Inverter(
    input A,
    output X
);
    nand(X,A,A) ; //GATE LEVEL
    assign X = !(A && A) ; //DATAFLOW

endmodule
```

testbench.sv

```
`default_nettype none

module nand_inverter ;
    reg i_a ;
    wire x ;

    NAND_Inverter calc(i_a, x) ;

    initial
    begin
        $dumpfile("dump.vcd") ;
        $dumpvars(0 , calc) ;

        $display("Using a 7400 IC as an inverter") ;
        #1
        i_a<=0 ;
        #1

        #1
        i_a<=1 ;
        #1

        $finish() ;
    end
endmodule

/*Inverter by using a single 7400 IC*/
```

LINK: <https://www.edaplayground.com/x/9LZD>

b.) Using a single 7400 IC as two-input AND gate.

design.sv

```
`default_nettype none

module Nand_as_and(
    input A,B,
    output X
);
    wire w1,w2;
    //GATE LEVEL MODELLING
    nand g1(w1,A,B);
    nand g2(X,w1,w1);
    //DATA FLOW MODELLING
    //assign X= !(((A && B)) && (!(A && B)));

endmodule
```

testbench.sv

```
`default_nettype none

module nand_as_and;

    reg i_a,i_b;
    wire out_x;

    Nand_as_and h_dut(i_a,i_b,out_x);

    // UPDATED UNIT TEST //

    initial
    begin
        $dumpfile("dump.vcd");
        $dumpvars(0, h_dut);

        $display("TESTING: A two-input AND, Using a single 7400 IC");
        $monitor(i_a,i_b,out_x);
        #1
        i_a <= 0;
        i_b <= 0;
        #1

        #1
        i_a <= 0;
```

```

    i_b <= 1;
    #1

    #1
    i_a <= 1;
    i_b <= 0;
    #1

    #1
    i_a <= 1;
    i_b <= 1;
    #1

    $finish();
end

```

endmodule

LINK: <https://www.edaplayground.com/x/72LX>

c.) Using a single 7400 IC as two-input OR gate.

design.sv

```

`default_nettype none

module Nand_as_or (
    input A,B,
    output X
);
    wire w1,w2;
    //GATE LEVEL MODELLING
    nand g1(w1,A,A);
    nand g2(w2,B,B);
    nand g3(X,w1,w2);
    //DATA FLOW MODELLING
    //assign w1 = !(A && A);
    //assign w2 = !(B && B);
    //assign X = !(w1 && w2);

endmodule

```

testbench.sv

```

`default_nettype none

module nand_as_or;

```

```

reg i_a,i_b;
wire out_x;

Nand_as_or h_dut(i_a,i_b,out_x);

// UPDATED UNIT TEST //

initial
begin
    $dumpfile("dump.vcd");
    $dumpvars(0, h_dut);

    $display("TESTING: A two-input OR, Using a single 7400 IC");
    $monitor(i_a,i_b,out_x);
    #1
    i_a <= 0;
    i_b <= 0;
    #1

    i_a <= 0;
    i_b <= 1;
    #1

    i_a <= 1;
    i_b <= 0;
    #1

    i_a <= 1;
    i_b <= 1;
    #1

    $finish();
end

endmodule

```

LINK: <https://www.edaplayground.com/x/kVFj>

d.) Using a single 7400 IC as two-input XOR gate.

design.sv

```
`default_nettype none
```

```

module Nand_as_xor (
    input A,B,
    output X
);
    wire C,D,E;
    //GATE LEVEL
    nand(C,A,B);
    nand(D,A,C);
    nand(E,C,B);
    nand(X,D,E);
    //DATA FLOW MODELLING
    // wire C=!(A&&B);
    // wire D=!(A&&C);
    // wire E=!(C&&B);
    // assign X=!(D&&E);
endmodule

```

testbench.sv

```

`default_nettype none

module nand_as_xor;

    reg i_a,i_b;
    wire out_x;

    Nand_as_xor h_dut(i_a,i_b,out_x);

    // UPDATED UNIT TEST //

    initial
        begin
            $dumpfile("dump.vcd");
            $dumpvars(0, h_dut);

            $display("TESTING: Nand as XOR using single 7400IC");

            #1
            i_a <= 0;
            i_b <= 0;

            #1
            i_a <= 0;
            i_b <= 1;

```

```
#1
i_a <= 1;
i_b <= 0;
```

```
#1
i_a <= 1;
i_b <= 1;
```

```
#1
$finish();
end
```

```
endmodule
```

LINK: <https://www.edaplayground.com/x/n7au>

3. Construct & record the output of circuit using HDL that implements the Boolean function:

$$F = A (B + C)$$

a) Construct the circuit using Logic gates & verify the truth table.

b) Construct the circuit using NAND gates only & verify the truth table.

design.sv

```
`default_nettype none
module obj_3(
    input A, B, C,
    output F
);
    wire w1,w2;

    //A. Using Logic Gates

    //GATE LEVEL
    or g1(w1,B,C);
    and g2(F,A,w1);
    //DATA FLOW
    //assign F = (A && (B || C)) ;
```

```
//B. Using NAND GATES ONLY
```

```
//B or C
```

```
//nand g1(w1,B,B);
```

```
//nand g2(w2,C,C);
```

```
//nand g3(X,w1,w2);
```

```
//A and (B or C)
```

```
//nand g4(w3,A,X);
```

```
//nand g5(F,w3,w3);
```

```
//DATA FLOW
```

```
//assign F = (A && (B || C)) ;
```

```
endmodule
```

testbench.sv

```
`default_nettype none
```

```
module Obj_3 ;
```

```
reg i_A, i_B, i_C ;
```

```
wire oF;
```

```
obj_3 OUTPUT(i_A, i_B, i_C, oF) ;
```

```
initial
```

```
begin
```

```
$dumpfile("dump.vcd") ;
```

```
$dumpvars(0 , OUTPUT) ;
```

```
$display("HDL program for objective 3, F=A(B+C)") ;
```

```
#1
```

```
i_A<=0 ;
```

```
i_B<=0 ;
```

```
i_C<=0 ;
```

```
#1
```

```
#1
```

```
i_A<=0 ;
```

```
i_B<=0 ;
```

```
i_C<=1 ;
```

```
#1
```

```
#1
```

```
i_A<=0 ;
```

```
i_B<=1 ;
```

```
i_C<=0 ;
```

```
#1
```

```

#1
i_A<=0 ;
i_B<=1 ;
i_C<=1 ;
#1

#1
i_A<=1 ;
i_B<=0 ;
i_C<=0 ;
#1

#1
i_A<=1 ;
i_B<=0 ;
i_C<=1 ;
#1

#1
i_A<=1 ;
i_B<=1 ;
i_C<=0 ;
#1

#1
i_A<=1 ;
i_B<=1 ;
i_C<=1 ;
#1

$finish() ;
end
endmodule


```

LINK: <https://www.edaplayground.com/x/NV4G>

Observation:


EP Wave for Obj.1

a.NAND Gate

 


The above EP Wave shows the truth table of NAND gate. Here when input A is 1 and B is 1 the output X is 0 which satisfies the working of the Nand Gate.

b.NOR Gate

 


The above EP Wave shows the truth table of NOR gate. Here when input A is 1 and B is 1 the output X is 0 which satisfies the working of the NOR Gate.

c.Hex Inverter

 


The above EP Wave shows the truth table of NOT gate. Here when input A is 1 the output X is 0 which satisfies the working of the Hex Inverter.

d.AND Gate

 


The above EP Wave shows the truth table of AND gate. Here when input A is 1 and B is 1 the output X is 1 which satisfies the working of the AND Gate.

e.OR Gate

 

The above EP Wave shows the truth table of OR gate. Here when input A is 1 and B is 1 the output X 1 is A which satisfies the working of the OR Gate.


f. XOR Gate

 

The above EP Wave shows the truth table of XOR gate. Here when input A is 1 and B is 1 the output X is 0 which satisfies the working of the XOR Gate.


EP Wave for Obj.2

a. An inverter

 


The above EP Wave shows the truth table of Hex Inverter using a NAND gate of 7400 IC, here when input A is 1 and B is 0 which satisfies the working of the Hex Inverter gate.

b. A two-input AND

 

The above EP Wave shows the truth table of AND gate using 2 NAND gates of a 7400 IC, here when input A is 1 and B is 1 the output X is 1 which satisfies the working of the AND gate.


c) A two-input OR.

 

The


above EP Wave shows the truth table of OR gate using 3 NAND gates of a 7400 IC, here when input A is 1 and B is 1 the output X is 1 which satisfies the working of the OR gate.

d) A two-input XOR.

 


The above EP Wave shows the truth table of XOR gate using 4 NAND gates of a 7400 IC, here when input A is 1 and B is 1 the output X is 0 which satisfies the working of the XOR gate.

EP Wave for Obj.3

 

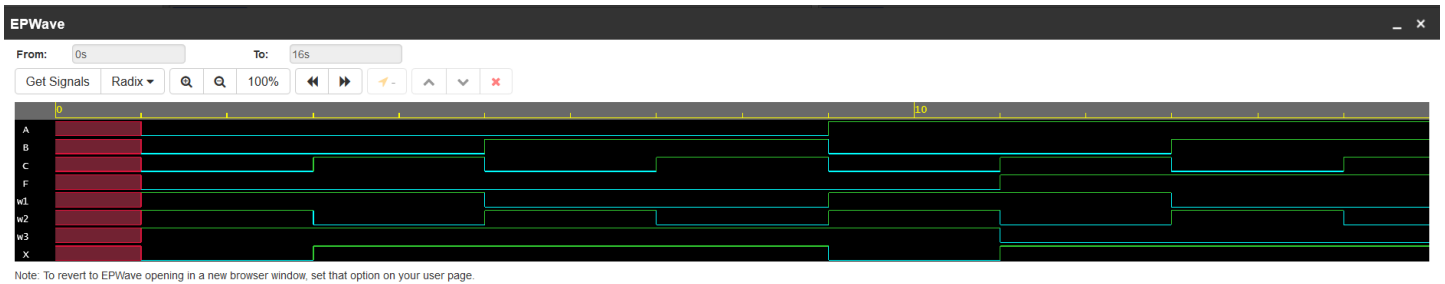a. To verify the above function $F=A(B+C)$ we have used 1 or gate and 1 AND gate. The above EP Wave verifies the boolean function, when input A is 0 , B is 1 & C is 1 and output F is 0.



b. To verify the above function $F=A(B+C)$ we have used 5 NAND gates. The above EP Wave verifies the boolean function, when input A is 1 , B is 1 & C is 0 and output F is 1.

Conclusion:

Hence, the logical behaviours of all the gates have been verified using HDL program in **Objective 1**. In **Objective 2**, we have concluded that all other gates such as AND,OR,XOR etc can be produced by using a single **7400IC Nand Gate**. In **Objective 3**, it can be concluded that output F can be constructed using NAND Gate. Thus the final output F has been recorded and truth table is also verified.

IV. POST LAB:

1. What is the voltage range for operation of digital circuits?

Ans: Voltage range for operations of Digital Circuits is 0V – 5V.

2. What is the significance of ground and VCC connection?

Ans: VCC is the higher voltage with respect to ground. VCC is the power input of a device. It may be positive or negative with respect to Ground. Ground is normally at zero volts or the zero voltage point for a power supply and circuit.

3. Which gates are known as universal gates & why?

Ans: NAND and NOR gates are known as universal gates which can be combined to form any other logic gates.

4. What is the minimum number of NAND gates used to realize an EXOR gate?

Ans: 4 NAND gates are used to realize an EXOR gate.